

# Question 1(a) [3 marks]

Define Active and Passive Components with example.

Answer:

Table: Active vs Passive Components

Component Type	Definition	Power	Examples
Active Components	Components that can amplify signals and control current flow	Can provide power gain	Transistor, Diode, IC
Passive Components	Components that cannot amplify signals	Cannot provide power gain	Resistor, Capacitor, Inductor

- **Active components:** Control and amplify electrical signals using external power
- **Passive components:** Store or dissipate energy without amplification

Mnemonic: "Active Amplifies, Passive Preserves"

# Question 1(b) [4 marks]


Explain construction and working of LDR.

Answer:

Construction:

- **Serpentine track** of cadmium sulfide on ceramic substrate
- **Metal electrodes** at both ends for connections
- **Protective coating** prevents moisture damage

Working Principle:

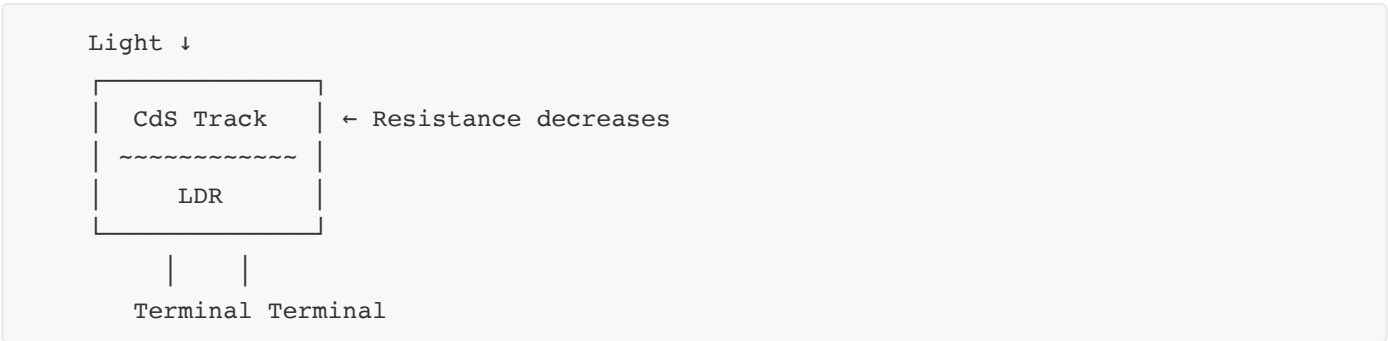

- **Light intensity ↑:** Resistance ↓ (conducts more)
- **Darkness:** Resistance ↑ (conducts less)
- **Applications:** Street lights, automatic cameras

**Mnemonic:** "Light Low Resistance"

## Question 1(c) [7 marks]


**Define Capacitance and explain Aluminum Electrolytic wet type capacitor.**

**Answer:**

**Capacitance Definition:**

Ability to store electrical charge.  $C = Q/V$  (Farads)

**Aluminum Electrolytic Capacitor:**

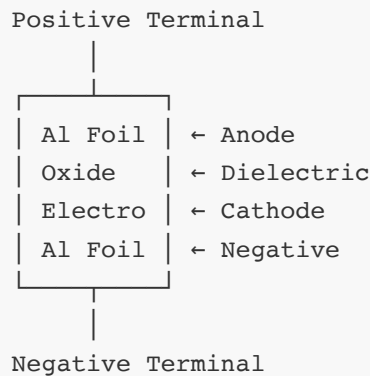

**Construction:**

- **Anode:** Aluminum foil with oxide layer
- **Dielectric:** Thin aluminum oxide film
- **Cathode:** Liquid electrolyte with aluminum foil
- **Polarity:** Must be connected correctly

**Features:**

- **High capacitance** values ( $1\mu\text{F}$  to  $10,000\mu\text{F}$ )
- **Polarized** - has positive and negative terminals
- **Applications:** Power supply filtering, coupling

**Mnemonic:** "Aluminum Always Amplifies"

## Question 1(c OR) [7 marks]

**Explain the color band coding method of Resistor. Write color band of  $32\ \Omega \pm 10\%$  resistance.**

**Answer:**

**Color Code Table:**

Color	Digit	Multiplier	Tolerance
Black	0	1	-
Brown	1	10	±1%
Red	2	100	±2%
Orange	3	1K	-
Yellow	4	10K	-
Green	5	100K	±0.5%
Blue	6	1M	±0.25%
Violet	7	10M	±0.1%
Gray	8	100M	±0.05%
White	9	1G	-
Silver	-	0.01	±10%
Gold	-	0.1	±5%

For 32 Ω ±10%:

Orange	Red	Gold	Silver
3	2	0.1	±10%
↓	↓	↓	↓
1st	2nd	Mult	Tol

Calculation:  $3 \times 2 \times 0.1 = 3.2 \times 10 = 32 \, \Omega$

Mnemonic: "Big Boys Race Our Young Girls But Violet Generally Wins"

Question 2(a) [3 marks]

Define following terms: 1) Rectifier 2) Ripple factor 3) Filter

Answer:

Term	Definition
Rectifier	Circuit that converts AC to pulsating DC
Ripple Factor	Ratio of AC component to DC component in output
Filter	Circuit that smooths pulsating DC to pure DC

- **Rectifier:** Uses diodes to allow current in one direction
- **Ripple factor:** Lower value means better filtering
- **Filter:** Uses capacitors/inductors to reduce ripples


**Mnemonic:** "Rectify Ripples, Filter Fixes"

## Question 2(b) [4 marks]

**Draw and explain positive clipper circuit with waveform.**

**Answer:**


**Circuit Diagram:**

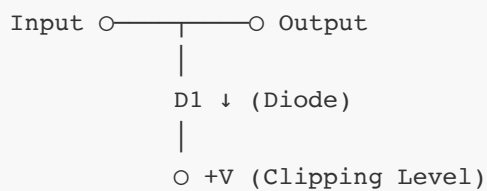

**Working:**

- **When  $V_{in} > +V$ :** Diode conducts, output = +V
- **When  $V_{in} < +V$ :** Diode off, output follows input
- **Result:** Clips positive peaks above +V level

**Waveform:**

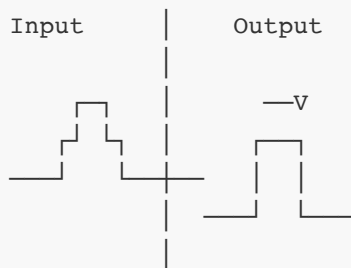

**Applications:** Signal limiting, protection circuits


**Mnemonic:** "Positive Peaks Prevented"

## Question 2(c) [7 marks]

**Explain working of full wave rectifier with two diodes.**

**Answer:**

**Circuit Diagram:**

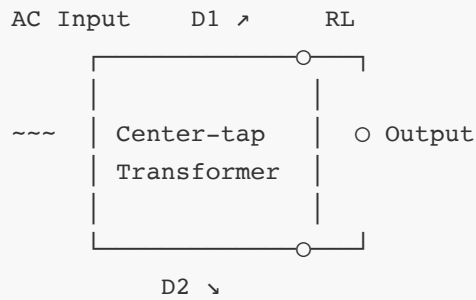**Working:**

- **Positive half-cycle:** D1 conducts, D2 off
- **Negative half-cycle:** D2 conducts, D1 off
- **Both diodes** work alternately
- **Output frequency** =  $2 \times$  input frequency

**Key Parameters:**

Parameter	Value
Peak Inverse Voltage	$2V_m$
Efficiency	81.2%
Ripple Factor	0.48
Form Factor	1.11

**Advantages:**

- **Better efficiency** than half-wave
- **Lower ripple** content
- **Higher transformer utilization**

**Mnemonic:** "Two Diodes, Two Halves"

## Question 2(a OR) [3 marks]

**Define rectifier and write its applications.**

**Answer:**

**Definition:**

Electronic circuit that converts alternating current (AC) into direct current (DC) using diodes.

**Applications:**

Application	Use
Power Supplies	DC voltage for electronic circuits
Battery Chargers	Converting AC mains to DC
DC Motors	Providing DC for motor drives
Electronic Devices	Laptops, phones, LED drivers

- **Primary function:** AC to DC conversion
- **Essential component:** In all electronic devices


**Mnemonic:** "Rectify AC, Deliver DC"

Question 2(b OR) [4 marks]

Explain working of Pi( $\pi$ ) type capacitor filter.

Answer:

Circuit Diagram:

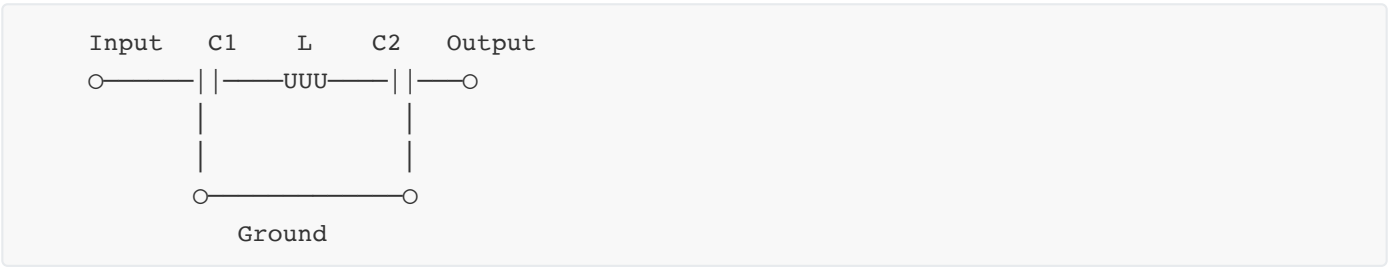

Working:

- **C1:** Filters initial ripples from rectifier
- **Inductor L:** Opposes current changes, smooths further
- **C2:** Final filtering for smooth DC output
- **Combined effect:** Excellent ripple reduction

Characteristics:

Parameter	Value
Ripple Factor	Very low ( $< 0.01$ )
Regulation	Good
Cost	Higher due to inductor
Applications	High-quality power supplies

Advantages:

- **Excellent filtering** performance
- **Low ripple** content
- **Good voltage regulation**

**Mnemonic:** "Pi Provides Perfect"

## Question 2(c OR) [7 marks]

Compare half wave and full wave bridge rectifier.


**Answer:**

**Comparison Table:**


Parameter	Half Wave	Full Wave Bridge
Diodes Required	1	4
Transformer	Simple	No center-tap needed
Efficiency	40.6%	81.2%
Ripple Factor	1.21	0.48
PIV	$V_m$	$V_m$
Output Frequency	$f$	$2f$
Transformer Utilization	28.7%	81.2%
Cost	Low	Moderate

**Circuit Diagrams:**

**Half Wave:**

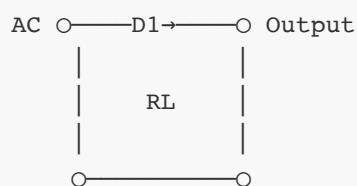

**Full Wave Bridge:**

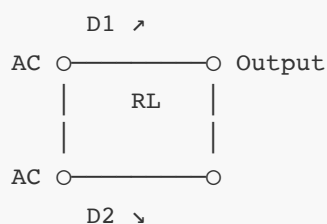

Key Differences:

- **Full wave:** Better efficiency and lower ripple
- **Half wave:** Simpler but poor performance
- **Bridge:** No center-tap transformer required

Mnemonic: "Half Wastes, Full Works"


Question 3(a) [3 marks]

Draw the symbols of following: 1) Zener diode 2) LED 3) Varactor diode


Answer:

Electronic Symbols:


Zener Diode:



LED:



Varactor Diode:

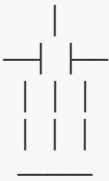

Symbol Details:

Component	Symbol Feature
Zener Diode	Normal diode with Z-shaped cathode
LED	Diode with arrows showing light emission
Varactor Diode	Diode with parallel lines (variable capacitor)

- **Zener:** Z indicates zener characteristics
- **LED:** Arrows show light output direction
- **Varactor:** Lines represent variable capacitance

Mnemonic: "Zener Zigs, LED Lights, Varactor Varies"


Question 3(b) [4 marks]

Explain construction and working of LED.

Answer:

Construction:

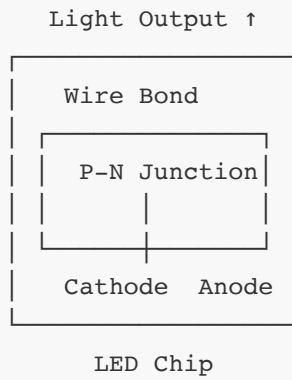

**Materials:**

- **P-type:** Boron-doped semiconductor
- **N-type:** Phosphorus-doped semiconductor
- **Common materials:** GaAs, GaP, GaN

**Working Principle:**

- **Forward bias:** Electrons recombine with holes
- **Energy release:** In form of photons (light)
- **Color:** Depends on semiconductor material and bandgap
- **Efficiency:** High light output with low power

**Applications:**

- **Indicators:** Status lights, displays
- **Lighting:** LED bulbs, strips
- **Electronics:** Seven-segment displays


**Mnemonic:** "Light Emitting, Energy Efficient"

## Question 3(c) [7 marks]

**Explain working characteristics of Zener diode.**

**Answer:**

**V-I Characteristics:**

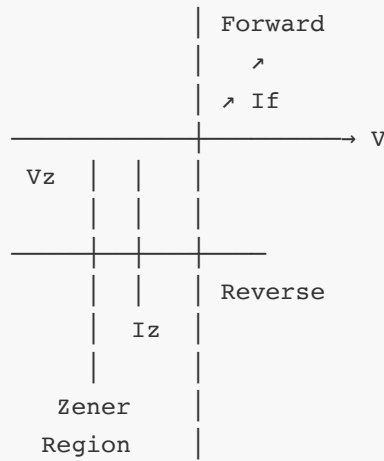

### Key Regions:

Region	Characteristics
Forward Bias	Normal diode operation (0.7V)
Reverse Bias	Small leakage current
Zener Region	Constant voltage ( $V_z$ )
Breakdown	Sharp voltage breakdown

### Important Parameters:

- **Zener Voltage ( $V_z$ ):** Breakdown voltage
- **Zener Current ( $I_z$ ):** Current in breakdown region
- **Maximum Power:**  $V_z \times I_{z(max)}$
- **Temperature coefficient:** Voltage variation with temperature

### Applications:

- **Voltage regulation:** Maintains constant output
- **Reference voltage:** Precise voltage source
- **Overvoltage protection:** Protects circuits

### Advantages:

- **Sharp breakdown:** Well-defined voltage
- **Low dynamic resistance:** Good regulation
- **Wide range:** Available in many voltages

**Mnemonic:** "Zener Zones Zero variation"

## Question 3(a OR) [3 marks]

Enlist the applications of varactor diode.

Answer:

Applications Table:

Application	Function
Voltage Controlled Oscillators	Frequency tuning with voltage
Automatic Frequency Control	Maintains oscillator frequency
Electronic Tuning	Radio/TV channel selection
Phase Locked Loops	Frequency synchronization
Frequency Multipliers	Harmonic generation
Parametric Amplifiers	Low-noise amplification

Key Features:

- **Voltage variable:** Capacitance changes with reverse voltage
- **No mechanical parts:** Electronic tuning only
- **Fast response:** Quick frequency changes

Mnemonic: "Voltage Varies Capacitance"

### Question 3(b OR) [4 marks]

Explain working of photo diode.

Answer:

Construction & Symbol:



Working Principle:

- **Light absorption:** Creates electron-hole pairs
- **Reverse bias:** Widens depletion region
- **Photocurrent:** Proportional to light intensity
- **Fast response:** Quick detection capability

Characteristics:

Parameter	Description
Dark Current	Current without light
Photocurrent	Current proportional to light
Responsivity	Current per unit light power
Response Time	Speed of detection

**Applications:**

- **Light sensors:** Automatic lighting systems
- **Optical communication:** Fiber optic receivers
- **Safety systems:** Smoke detectors
- **Solar panels:** Light to electrical energy


**Mnemonic:** "Photo Produces Proportional current"

## Question 3(c OR) [7 marks]

**Explain Zener diode as a voltage regulator.**

**Answer:**

**Voltage Regulator Circuit:**

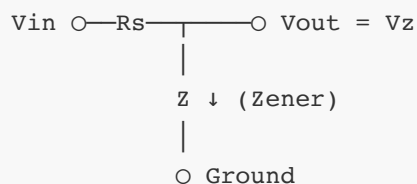**Working Principle:**

- **Zener operates** in breakdown region
- **Output voltage** remains constant at  $V_z$
- **Series resistor  $R_s$**  limits current
- **Load changes** don't affect output voltage

**Design Equations:**

Parameter	Formula
Series Resistance	$R_s = (V_{in} - V_z) / I_z$
Load Current	$I_L = V_z / R_L$
Zener Current	$I_z = I_s - I_L$
Power Dissipation	$P_z = V_z \times I_z$

**Regulation Characteristics:**

- **Line regulation:** Output change with input variation
- **Load regulation:** Output change with load variation
- **Efficiency:** Generally low due to Zener power loss

**Advantages:**

- **Simple circuit:** Few components required
- **Good regulation:** Stable output voltage
- **Fast response:** Quick voltage correction

**Limitations:**

- **Poor efficiency:** Power wasted in Zener
- **Limited current:** Cannot supply high currents
- **Temperature sensitivity:** Voltage varies with temperature

**Applications:**

- **Reference voltage:** Precise voltage source
- **Simple regulators:** Low current applications
- **Protection circuits:** Overvoltage protection

**Mnemonic:** "Zener Zones provide Zero variation"

## Question 4(a) [3 marks]


---

**Draw the symbol and construction of PNP and NPN transistor with proper notation.**


**Answer:**

**Transistor Symbols:**


NPN Transistor:

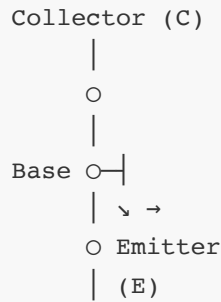


PNP Transistor:

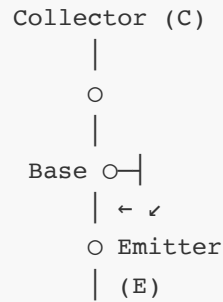**Construction Diagrams:**

NPN Structure:

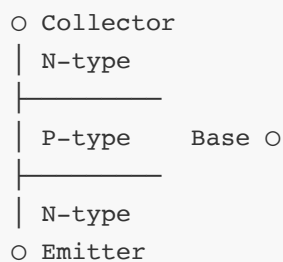


PNP Structure:

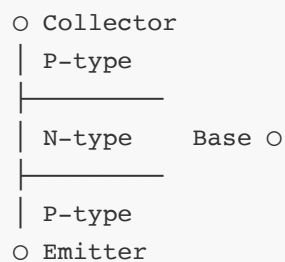
**Terminal Identification:**

- **Emitter:** Heavily doped, arrow shows current direction
- **Base:** Thin, lightly doped middle region
- **Collector:** Moderately doped, collects charge carriers


**Current Direction:**

- **NPN:** Arrow points outward (emitter to base)
- **PNP:** Arrow points inward (base to emitter)

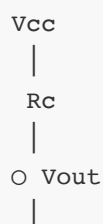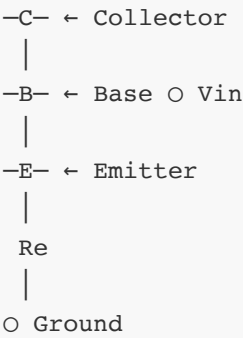
**Mnemonic:** "NPN: Not Pointing iN, PNP: Pointing iN Please"**Question 4(b) [4 marks]****Draw and Explain characteristics of CE amplifier.****Answer:****CE Amplifier Circuit:**



Input Characteristics (IB vs VBE):

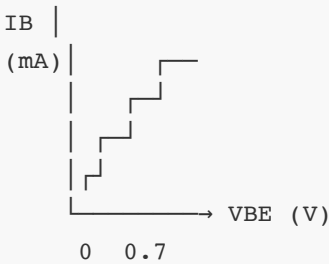

Output Characteristics (IC vs VCE):

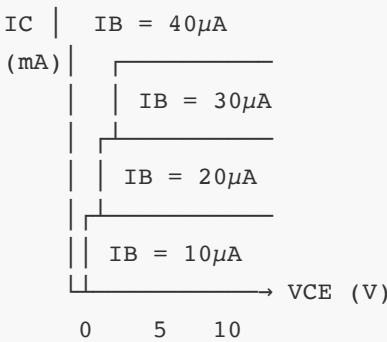

Key Features:

Parameter	CE Configuration
Current Gain	$\beta = I_C/I_B$ (high)
Voltage Gain	High
Power Gain	Very high
Input Impedance	Medium
Output Impedance	High
Phase Shift	180°

Regions of Operation:

- **Cut-off:** Both junctions reverse biased

- **Active:** BE forward, BC reverse biased
- **Saturation:** Both junctions forward biased

**Mnemonic:** "Common Emitter, Current Enlarged"

## Question 4(c) [7 marks]

Derive relation between current gains  $\alpha$ ,  $\beta$  and  $\gamma$ .

**Answer:**

**Current Gain Definitions:**

Gain	Configuration	Formula
$\alpha$ (Alpha)	Common Base	$\alpha = I_C/I_E$
$\beta$ (Beta)	Common Emitter	$\beta = I_C/I_B$
$\gamma$ (Gamma)	Common Collector	$\gamma = I_E/I_B$

**Derivation:**

### Step 1: Basic Current Relation

$I_E = I_B + I_C$  ... (Kirchhoff's Current Law)

### Step 2: Express $I_C$ in terms of $I_E$

$\alpha = I_C/I_E$

Therefore:  $I_C = \alpha \times I_E$  ... (1)

### Step 3: Substitute in current equation

$I_E = I_B + \alpha \times I_E$

$I_E - \alpha \times I_E = I_B$

$I_E(1 - \alpha) = I_B$

$I_E = I_B/(1 - \alpha)$  ... (2)

### Step 4: Find $\beta$

$\beta = I_C/I_B$

From (1):  $I_C = \alpha \times I_E$

From (2):  $I_E = I_B/(1 - \alpha)$

Therefore:  $I_C = \alpha \times I_B/(1 - \alpha)$

### Step 5: Final relation for $\beta$

$\beta = I_C/I_B = \alpha/(1 - \alpha)$  ... (3)

### Step 6: Express $\alpha$ in terms of $\beta$

From equation (3):

$\beta(1 - \alpha) = \alpha$

$\beta - \beta\alpha = \alpha$

$\beta = \alpha + \beta\alpha = \alpha(1 + \beta)$

Therefore:  $\alpha = \beta/(1 + \beta)$  ... (4)



**Step 7: Find  $\gamma$** 

$$\gamma = I_E / I_B$$

$$\text{From (2): } \gamma = 1 / (1 - \alpha)$$

Substituting  $\alpha$  from (4):

$$\gamma = 1 / (1 - \beta / (1 + \beta))$$

$$\gamma = (1 + \beta) / (1 + \beta - \beta)$$

$$\gamma = 1 + \beta \dots (5)$$

**Final Relations:**

Relation	Formula
$\beta$ in terms of $\alpha$	$\beta = \alpha / (1 - \alpha)$
$\alpha$ in terms of $\beta$	$\alpha = \beta / (1 + \beta)$
$\gamma$ in terms of $\beta$	$\gamma = 1 + \beta$
Verification	$\alpha + \beta \times \alpha = \beta$

**Typical Values:**

- $\alpha \approx 0.98$  to  $0.995$
- $\beta \approx 50$  to  $200$
- $\gamma \approx 51$  to  $201$

**Mnemonic:** "Alpha Beta Gamma, Always Better Gains"

**Question 4(a OR) [3 marks]**

**Define Active, Saturation and Cut-off region for transistor amplifier.**

**Answer:**

**Operating Regions:**

Region	Base-Emitter	Base-Collector	Characteristics
<b>Active</b>	Forward Biased	Reverse Biased	Amplification region
<b>Saturation</b>	Forward Biased	Forward Biased	Switch ON state
<b>Cut-off</b>	Reverse Biased	Reverse Biased	Switch OFF state

**Detailed Description:****Active Region:**

- **Normal amplification** mode
- **$I_C = \beta \times I_B$**  relationship holds
- **Linear operation** for small signals

**Saturation Region:**

- **Both junctions** forward biased
- **Maximum collector current** flows
- **VCE  $\approx$  0.2V** (very low)
- **Used in switching** applications

**Cut-off Region:**

- **No base current** ( $I_B = 0$ )
- **No collector current** ( $I_C = 0$ )
- **Transistor acts** like open switch

**Mnemonic:** "Active Amplifies, Saturated Switches, Cut-off Cuts"


## Question 4(b OR) [4 marks]

---

**Explain working of Transistor as an amplifier.**

**Answer:**

**Amplifier Circuit:**

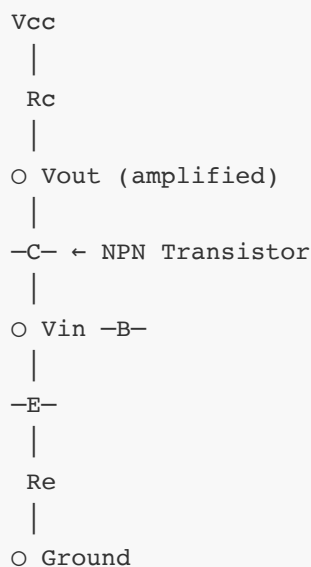**Working Principle:**

- **Small input signal** applied to base-emitter
- **Input resistance** is low (few  $k\Omega$ )
- **Small base current** controls large collector current
- **Output taken** from collector-emitter
- **Current amplification:**  $I_C = \beta \times I_B$

**Amplification Process:**

Parameter	Input	Output
Signal Level	Small	Large
Current	$\mu\text{A}$ range	mA range
Voltage	mV range	V range
Power	$\mu\text{W}$ range	mW range

**Key Features:**

- **Current gain:**  $\beta$  (50-200 typical)
- **Voltage gain:** Depends on load resistance
- **Power gain:** Product of current and voltage gains
- **Phase inversion:**  $180^\circ$  in CE configuration

**Applications:**

- **Audio amplifiers:** Music systems
- **RF amplifiers:** Radio transmitters
- **Op-amp stages:** Integrated circuits

**Mnemonic:** "Tiny signal Triggers Tremendous output"

## Question 4(c OR) [7 marks]

---

Compare CB, CC, and CE amplifier configuration.


Answer:

Comprehensive Comparison:

Parameter	Common Base (CB)	Common Emitter (CE)	Common Collector (CC)
Input Terminal	Emitter	Base	Base
Output Terminal	Collector	Collector	Emitter
Common Terminal	Base	Emitter	Collector
Current Gain	$\alpha < 1$	$\beta \gg 1$	$\gamma = (1 + \beta)$
Voltage Gain	High	High	$< 1 (\approx 1)$
Power Gain	Medium	Very High	Medium
Input Resistance	Very Low (20-50 $\Omega$ )	Medium (1-5k $\Omega$ )	Very High (100k $\Omega$ )
Output Resistance	Very High (1M $\Omega$ )	High (50k $\Omega$ )	Low (25 $\Omega$ )
Phase Shift	0°	180°	0°
Frequency Response	Excellent	Good	Good
Applications	RF Amplifiers	Audio Amplifiers	Buffer, Impedance Matching

Circuit Diagrams:

Common Base:

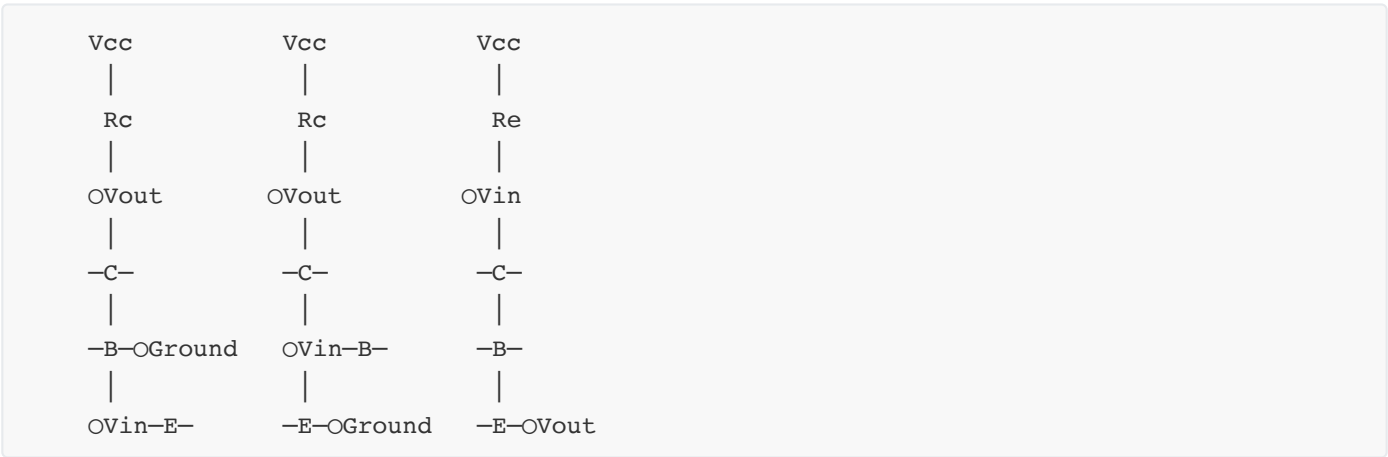

Key Characteristics:

Common Base (CB):

- **High frequency** performance
- **No current gain** but high voltage gain
- **Input-output isolation** excellent
- **Used in:** RF amplifiers, high-frequency circuits

**Common Emitter (CE):**

- **Most popular** configuration
- **High current and voltage** gain
- **Good compromise** of all parameters
- **Used in:** Audio amplifiers, general amplification

**Common Collector (CC):**

- **Unity voltage gain** (voltage follower)
- **High current gain**
- **Impedance transformation** (high to low)
- **Used in:** Buffer amplifiers, impedance matching

**Selection Criteria:**

Application	Best Configuration	Reason
High Frequency	CB	Excellent frequency response
General Amplification	CE	High power gain
Buffer/Isolation	CC	High input, low output impedance
Power Amplifiers	CE	Maximum power gain


**Mnemonic:** "CB for Communication, CE for Common use, CC for Coupling"

**Question 5(a) [3 marks]**

**Draw the pin diagram of IC 555.**

**Answer:**

**IC 555 Pin Diagram:**

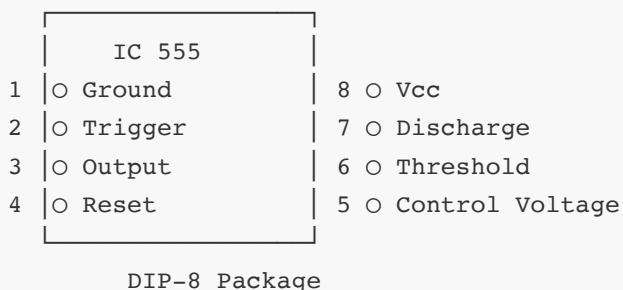

**Pin Functions:**

Pin	Name	Function
1	Ground	0V reference
2	Trigger	Start timing cycle
3	Output	Timer output
4	Reset	Master reset (active low)
5	Control	Voltage reference control
6	Threshold	Stop timing cycle
7	Discharge	Timing capacitor discharge
8	Vcc	Power supply (+5V to +18V)

Key Points:

- **Dual-in-line** 8-pin package
- **Power supply:** 5V to 18V DC
- **Output current:** Up to 200mA
- **Reset pin:** Normally connected to Vcc

Mnemonic: "Great Timer, Great Pins"

Question 5(b) [4 marks]

List out Features of 555 Timer IC.

Answer:

Key Features:

Feature	Specification
Supply Voltage	5V to 18V
Output Current	200mA source/sink
Temperature Range	0°C to 70°C
Timing Range	µs to hours
Accuracy	±1% typical
Modes	Monostable, Astable, Bistable

Technical Features:

- **CMOS/TTL compatible** output levels

- **High current** output capability
- **Wide supply voltage** range
- **Temperature stable** operation

#### Functional Features:

- **Three operating modes** available
- **External timing** components
- **Reset capability** for control
- **Low power consumption** design

#### Advantages:

- **Versatile timer** for multiple applications
- **Easy to use** with minimal external components
- **Reliable operation** in various conditions


**Mnemonic:** "Fantastic Features, Flexible Functions"

## Question 5(c) [7 marks]

Explain Mono stable multivibrator using 555 timer IC.

**Answer:**

**Monostable Circuit:**

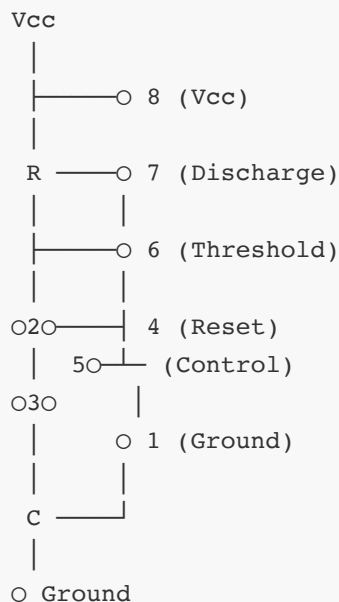

**Working Principle:**

**Stable State:**

- **Output LOW** (approximately 0V)

- **Capacitor discharged** through pin 7
- **Threshold voltage** below  $V_{cc}/3$

**Triggered State:**

- **Negative pulse** applied to trigger (pin 2)
- **Output goes HIGH** immediately
- **Discharge transistor** turns OFF
- **Capacitor starts** charging through R

**Timing Period:**

- **Duration:**  $T = 1.1 \times R \times C$
- **Output remains HIGH** for calculated time
- **Automatic return** to stable state

**Return to Stable:**

- **Capacitor voltage** reaches  $2V_{cc}/3$
- **Threshold triggered** (pin 6)
- **Output returns** to LOW
- **Discharge begins** again

**Key Characteristics:**

Parameter	Description
Pulse Width	$T = 1.1 RC$
Trigger Level	$V_{cc}/3$
Threshold Level	$2V_{cc}/3$
Output High	$\sim V_{cc} - 1.5V$
Output Low	$\sim 0.1V$

**Applications:**

- **Pulse generation:** Fixed width pulses
- **Time delays:** Switch-on delays
- **Missing pulse detection:** Watchdog timers
- **Debouncing circuits:** Switch contact cleaning

**Design Example:**

For  $T = 1ms$ : If  $C = 0.1\mu F$ , then  $R = 9.1k\Omega$

**Mnemonic:** "Mono means One pulse Only"



## Question 5(a OR) [3 marks]

List out applications of IC 555.

Answer:

Timer Applications:

Category	Applications
Timing Circuits	Delay timers, Pulse generators
Oscillators	Clock generators, Frequency dividers
Control Circuits	PWM controllers, Motor speed control
Detection	Missing pulse detectors, Burglar alarms
Communication	Tone generators, Frequency shift keying
Automotive	Turn signal flashers, Windshield wipers

Mode-wise Applications:

Monostable Mode:

- **Time delays** in circuits
- **Pulse width** generation
- **Debouncing** switches

Astable Mode:

- **LED flashers** and blinkers
- **Clock signals** generation
- **Tone generation** for buzzers

Bistable Mode:

- **Flip-flop** circuits
- **Memory elements**
- **Latch circuits**

Common Projects:

- **Electronic dice** using LEDs
- **Traffic light** controllers
- **Digital clocks** and timers


**Mnemonic:** "Timer for Tremendous Tasks"

## Question 5(b OR) [4 marks]

Draw and explain the internal block diagram of IC 555.

Answer:

Internal Block Diagram:

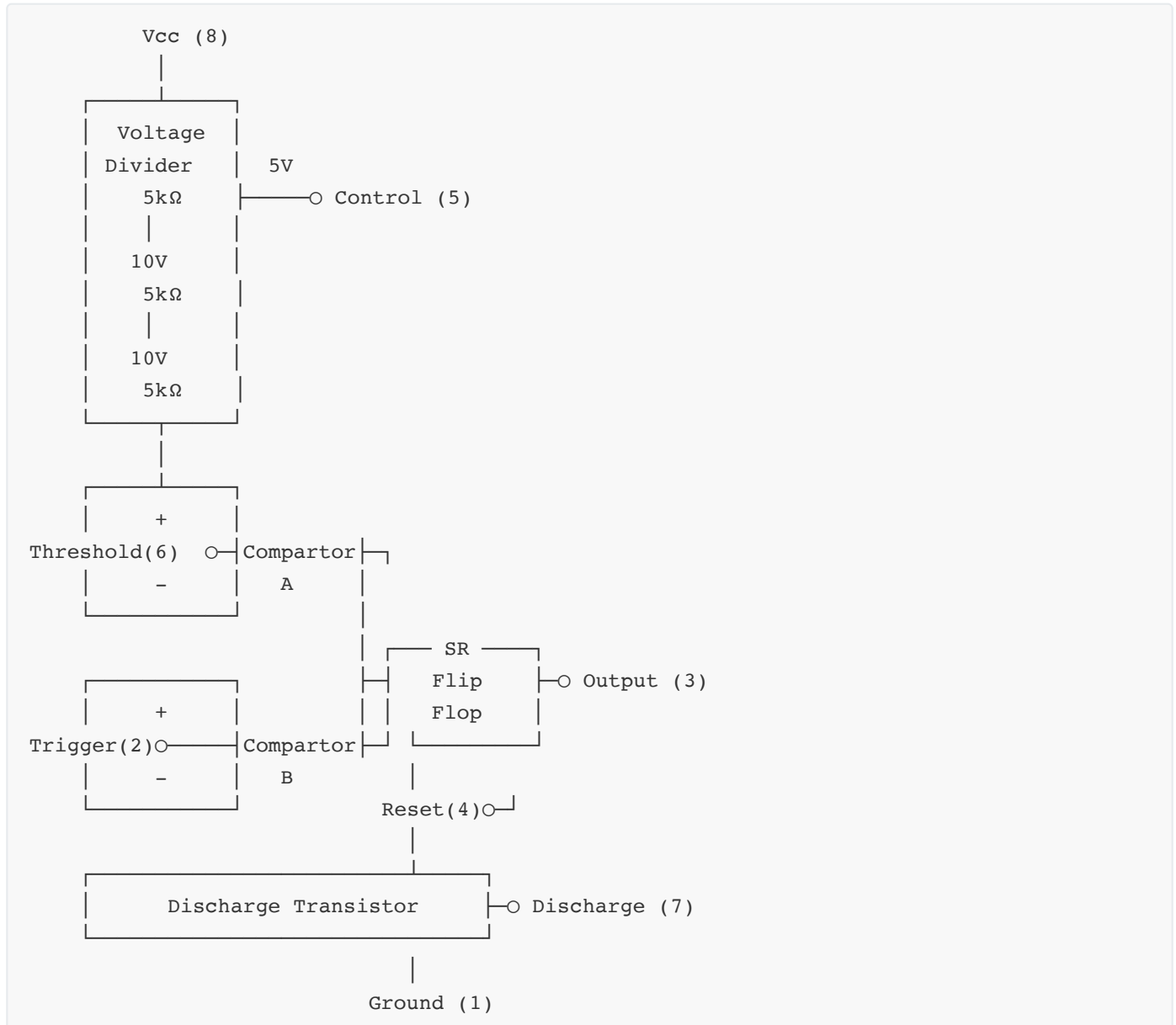

Block Functions:

Block	Function
Voltage Divider	Creates $V_{cc}/3$ and $2V_{cc}/3$ references
Comparator A	Compares threshold with $2V_{cc}/3$
Comparator B	Compares trigger with $V_{cc}/3$
SR Flip-Flop	Controls output state
Discharge Transistor	Discharges timing capacitor
Output Buffer	Provides high current output

Working:

- **Comparators** set and reset flip-flop
- **Output buffer** amplifies flip-flop output
- **Discharge transistor** controlled by flip-flop
- **Reference voltages** set trigger levels


**Mnemonic:** "Internal Intelligence, Integrated Implementation"

Question 5(c OR) [7 marks]

Explain astable multivibrator using 555 timer IC.

Answer:

Astable Circuit:

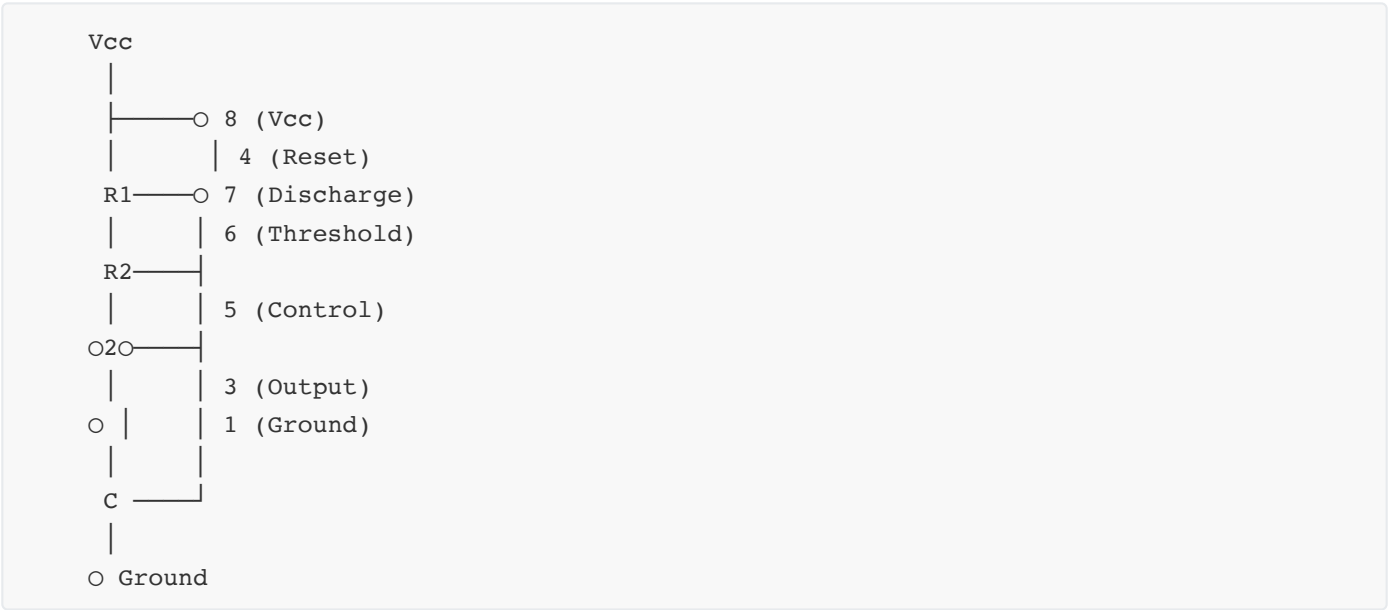

Working Principle:

Charging Phase:

- **Capacitor charges** through  $R1 + R2$
- **Output HIGH** during charging
- **Charging time:**  $T1 = 0.693(R1 + R2)C$
- **Voltage rises** from  $V_{cc}/3$  to  $2V_{cc}/3$


#### Discharging Phase:

- **Capacitor discharges** through  $R2$  only
- **Output LOW** during discharging
- **Discharging time:**  $T2 = 0.693 \times R2 \times C$
- **Voltage falls** from  $2V_{cc}/3$  to  $V_{cc}/3$

#### Frequency Calculations:

Parameter	Formula
Time HIGH	$T1 = 0.693(R1 + R2)C$
Time LOW	$T2 = 0.693 \times R2 \times C$
Total Period	$T = T1 + T2 = 0.693(R1 + 2R2)C$
Frequency	$f = 1.44/[(R1 + 2R2)C]$
Duty Cycle	$D = (R1 + R2)/(R1 + 2R2) \times 100\%$

#### Waveforms:

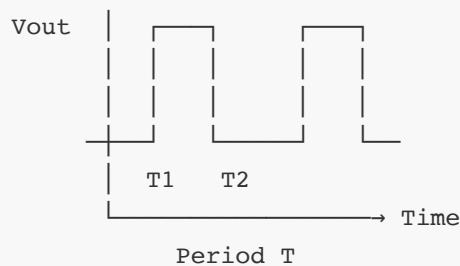

#### Design Example:

For  $f = 1\text{kHz}$ ,  $D = 60\%$ :

- Choose  $C = 0.1\mu\text{F}$
- Calculate  $R1 = 7.2\text{k}\Omega$ ,  $R2 = 3.6\text{k}\Omega$

#### Key Features:

- **Continuous oscillation** without external trigger
- **Frequency adjustable** by  $R$  and  $C$  values
- **Duty cycle** always  $> 50\%$  in basic circuit
- **Stable operation** over wide temperature range

### Applications:

- **LED flashers** and blinkers
- **Clock generators** for digital circuits
- **Tone generators** for alarms
- **PWM signal** generation

### Modifications for 50% Duty Cycle:

- **Add diode** in parallel with R2
- **Separate paths** for charge and discharge
- **Equal charge/discharge** times possible

**Mnemonic:** "Astable Always Alternates Automatically"